

# electronic design

# POWER


Technologies

Design Hotspots

Design Resources

Print Edition

More

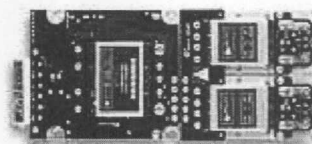[Click to view this week's ad screen](#)


## VIPAC Power System


[Reprints](#)

[Printer-Friendly](#)

[Email this Article](#)

[RSS](#)

[Submit](#)

[Font Size](#)

[What's This?](#)

[Ideas For Design]

## Microcontroller Interface Delivers Standard 4- To 20-mA Output

 R. Jayapal | [ED Online ID #17297](#) | [October 25, 2007](#)

**Power Management Solutions**

**It's ready for your close up.**

Voltage-to-current converters that feed grounded loads are common in industrial measurement and control applications. The conventional "textbook" circuit uses both positive and negative supply rails.

An earlier article by this author titled "Voltage-To-Current Converter Works From A Single Supply Rail" (Electronic Design, Feb. 17, 2003, ED Online 2985) described a circuit that could power grounded loads and needed only a positive supply rail. In a microcontroller-based application, a designer can use a digital-to-analog converter (DAC) to convert the digital data into an analog

voltage and use it to create a 4- to 20-mA current output.

But [Figure 1](#) shows a better way to generate an industry-standard 4- to 20-mA current output from 8-bit data (00â??FF) in a microcontroller-based system. This simple circuit uses a digital potentiometer (AD5260) driven by the microcontroller's serial peripheral interface (SPI) output.

Under ideal conditions, the voltages at the LM124 op amp's inputs (inverting and non-inverting) are the same:

$$V - iR_1 = V - I(R_2 + R_V).$$

where  $i$  is the current through the ground-referenced load;  $I$  is the current through the digital

**vicorpower.**

**VIPAC  
Power  
System**

potentiometer as set by constant current source; and  $R_V$  is the potentiometer resistance between the wiper and one end.

Solving for  $i$ :

$$i = [I(R_2 + R_V)/R_1]$$

In the example,  $I$  is selected as 0.08 mA,  $R_1$  is 100  $\Omega$ , and  $R_2$  is 5000  $\Omega$ . Also, the AD5260 digital potentiometer's total resistance is 20 k $\Omega$ .

Hence:

$$i = [(0.08 \text{ mA})(5000 + R_V)]/100$$

Using a routine in the microcontroller, load 00 to the digital potentiometer through the SPI, which drives the wiper to one end so that  $R_V$  is zero.

That makes:

$$i = 0.08 \times 10^{-5} (5000) = 0.004 \text{ A,} \\ \text{or 4 mA}$$

Load FF into the digital potentiometer and the wiper goes to the other end so that  $R_V$  is 20 k $\Omega$ . Therefore:

$$i = 0.08 \times 10^{-5} (5000 + 20,000) \\ = 0.020 \text{ A, or 20 mA}$$

As a result, for the data 00 to FF, the load current varies linearly from 4 mA to 20 mA.

However, the digital potentiometer's wiper resistance is significant even when  $R_V$  is low, which introduces an error. To eliminate this error, the digital potentiometer is connected as a voltage divider, with the wiper resistance in series with the op amp's non-inverting input.

If a 0.08-mA current source isn't readily available, you can use a National Semiconductor LM134 three-terminal adjustable current source and a potentiometer (VR1) to precisely set  $I$  at 0.08 mA (Fig. 2). Similarly, if a precise 5000- $\Omega$  resistance is unavailable for  $R_2$ , a 10-k $\Omega$  multi-turn potentiometer can be employed.

The advantage of this circuit is its simplicity and the fact that it uses only three of the microcontroller's port lines (SPI), unlike a DAC, which requires eight port lines for the 8-bit data. The circuit uses only a positive supply rail for operation. Digital potentiometers also are available with I2C interfaces, with integrated op amps, and with different resistance values. Designers can adapt this circuit for use with these digital potentiometers.



Reprints Printer-Friendly Email this Article RSS Submit Font Size ? What's This?

## POST YOUR COMMENTS HERE

Name:

Email:

### Search Electronic D



DRILL DEEPER:

### Email Newsletter

Sponsored By:



The Find Power Products newsletter brings you the new developments within the power design. The newsletter excerpts from industry leader Davis's exclusive blog, as well as overviews of the latest new

Enter Email to Subscribe

It's ready for  
your close up

### Top Viewed Article:

- [Build A Smart Battery \(A Single-Transistor Circuit\)](#)
- [Go Green With 100-W Audio Power Amplifiers](#)
- [Inside iPod](#)
- [Voltage-To-Current Converter From A Single-Supply](#)
- [Battery ICs Charge, Get Authenticate](#)

Your Comments:

Enter the text from the image below



Please refresh the page if you have trouble reading this text.

**SUBMIT**

#### FEATURED SPONSOR LINKS

##### **Innovative Triple/Quad PCI Express, Hot-Plug Controllers**

The new MAX5957-MAX5960 fully integrated hot-plug controllers allow safe insertion and removal of PCI Express (PCIe) cards from live PCI Express hot-plug slots. A flexible power-control schema reduces overall system cost. [Learn more.](#)

##### **New UCD9240 Fusion Digital Power(tm) Point-of-Load controller from Texas Instruments**

Gives designers faster time to market without sacrificing features or performance. This flexible and adaptable multi-rail controller provides high power density, dynamic power supply, load-optimized phase management and configurable sequencing.

##### **Power Electronics Technology Exhibition & Conference Oct. 30-Nov.1, Dallas, TX**

More Content. More Exhibitors. Refocused on the needs of electronic designers, it provides an educational program of seminars, technical sessions and professional advancement courses making it the power electronics industry's leading information event.


##### **findpowerproducts.com**

An online power-management product database Updated monthly, findpowerproducts.com currently has over 20,000 products introduced or revised from January 2002 to the present, with company data sheets, tutorials and descriptions of power-management functions.
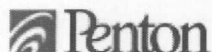
##### **Power Management that Matters**


Get more out of your power budget with the Freescale Power Management Portfolio. Integrate multiple functions on one chip and reduce board space and power consumption thanks to our SMARTMOS(TM) technology. [Learn more at freescale.com/powermanagement](#)

Electronic Design Europe ■■■ Electronic Design China ■■■ EEPN ■■■ Power Electronics ■■■ Auto Electronics ■■■ Microwaves & RF ■  
Schematics ■■■ Find Power Products ■■■ Military Electronics ■■■ Featured Vendors ■■■ EE Events ■■■ Free Design Resou




[Planet EE Network](#) | [Contact Us](#) | [Editorial Calendar](#) | [Media Kit](#) | [Submit Articles](#) | [Headlines](#) | [Site Feedback](#) |  
[Advanced Search](#) | [Help](#) | [Site Map](#)

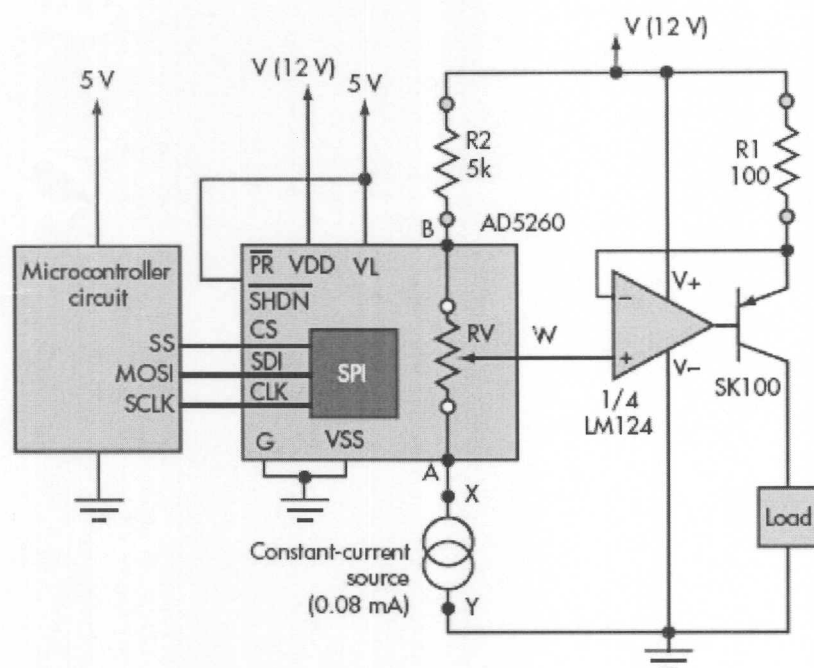Copyright © 2007 Penton Media, Inc., All rights reserved. [Privacy](#)



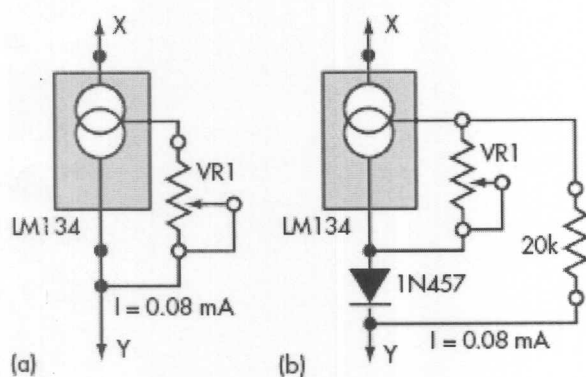**1. This simple circuit converts the digital output of a microcontroller's SPI to an analog voltage and uses it to generate a 4- to 20-mA current.**



2. An adjustable current source and 2-k $\Omega$  potentiometer can be used in place of the fixed 0.08-mA constant-current source (a). The current source can also be adapted for use in an application with varying ambient temperature by adding a diode and 20-k $\Omega$  resistor.